

# Gate-level Minimization

CS207 Lecture 3

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering  
Southern University of Science and Technology

Mar. 5, 2021



南方科技大学  
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY



# Gate-level minimization

- The complexity of digital logic gates to implement a Boolean function is directly related to the complexity of algebraic expression.
- Gate-level minimization is the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.
  - Difficult by hand for more than few inputs.
  - Typically by computer, need to understand the underlying principle.

# The map method



- The map method, first proposed by Veitch and slightly improvised by Karnaugh, provides a simple, straightforward procedure for the simplification of Boolean functions.
  - Called *Karnaugh map*.
- The map is a diagram consisting of *squares*. For  $n$  variables on a Karnaugh map there are  $2^n$  numbers of squares.
  - Each square or cell represents one of the minterms.
  - Since any Boolean function can be expressed as a sum of minterms, it is possible to recognize a Boolean function graphically in the map from the area enclosed by those squares whose minterms appear in the function.

# Two-variable K-map

- A two-variable system can form four minterms

		<i>B</i>	
		0	1
<i>A</i>	0	$m_0$	$m_1$
	1	$m_2$	$m_3$

		<i>B</i>	
		0	1
<i>A</i>	0	$A'B'$	$A'B$
	1	$AB'$	$AB$

		<i>B</i>	
		0	1
<i>A</i>	0	0	1
	1	1	1

- The two-variable Karnaugh map is a useful way to represent any of the 16 Boolean functions.
  - Example:
$$\begin{aligned}A + B &= A(B + B') + B(A + A') \\ &= AB + AB' + AB + A'B = AB + AB' + A'B\end{aligned}$$
- So the squares corresponding to  $AB$ ,  $AB'$ , and  $A'B$  are marked with 1.

# Three-variable K-map

- Since there are eight minterms for three variables, the map consists of eight cells or squares.
  - Minterms are arranged, not according to the binary sequence, but according to the sequence similar to the gray code.
  - **Between two consecutive rows or columns, only one single variable changes its logic value from 0 to 1 or from 1 to 0.**

		$BC$			
		00	01	11	10
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

# Three-variable K-map



- To understand the usefulness of the map for simplifying the Boolean functions, we must observe the basic properties of the adjacent squares.
  - Any two adjacent squares in the Karnaugh map differ by only one variable, which is complemented in one square and uncomplemented in one of the adjacent squares.
  - The sum of two minterms can be simplified to a single AND term consisting of less number of literals.
  - $m_1 + m_5 = A'B'C + AB'C = (A' + A)B'C = B'C$

		$BC$			
		00	01	11	10
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

# Three-variable K-map

- Example: Simplify the Boolean function  $F = A'BC + A'BC' + AB'C' + AB'C$ .

		$BC$			
		00	01	11	10
$A$	0	0	0	1	1
	1	1	1	0	0

- The first row:  $A'BC + A'BC' = A'B$ .
- The second row:  $AB'C' + AB'C = AB'$ .
- $F = A'B + AB'$ .

# Three-variable K-map

- Example: Simplify the Boolean function  $F = A'BC + AB'C' + ABC + ABC'$ .

		$BC$			
		00	01	11	10
$A$	0	0	0	1	0
	1	1	0	1	1

- The third column:  $A'BC + ABC = BC$ .
- The second row:  $AB'C' + ABC' = AC'$ .
- $F = BC + AC'$ .



# Three-variable K-map

- Example: Simplify the Boolean function  $F = \sum(1, 2, 3, 5, 7)$ .

		$BC$			
		00	01	11	10
$A$	0	0	1	1	1
	1	0	1	1	0

- $F = C + A'B$ .

# Three-variable K-map



- Example: Simplify the Boolean function  $F = \sum(0, 2, 4, 5, 6)$ .

		$BC$			
		00	01	11	10
$A$	0	1	0	0	1
	1	1	1	0	1

- $F = C' + AB'$ .

# Four-variable K-map

- Similar to the method used for two-variable and three-variable Karnaugh maps, four-variable Karnaugh maps may be constructed with 16 squares consisting of 16 minterms.

		$cd$			
		00	01	11	10
$ab$	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

# Four-variable K-map



- Two, four, or eight adjacent squares can be combined to reduce the number of literals in a function.
- The squares of the top and bottom rows as well as leftmost and rightmost columns may be combined.
  - When two adjacent squares are combined, it is called a *pair* and represents a term with three literals.
  - Four adjacent squares, when combined, are called a *quad* and its number of literals is two.
  - If eight adjacent squares are combined, it is called an *octet* and represents a term with one literal.
  - If, in the case all sixteen squares can be combined, the function will be reduced to 1.

# Four-variable K-map



- Example: Simplify the Boolean function  
 $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$ .
  - $A'B'C'D + A'BC'D = A'C'D$ ,
  - $ABC'D' + ABC'D = ABC'$ ,
- $F = A'C'D + ABC' + ACD + AB'C$ .
- This reduced expression is not a unique one.
  - If pairs are formed in different ways, the simplified expression will be different.

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	0	1	0	0
	01	0	1	0	0
	11	1	1	1	0
	10	0	0	1	1

# Four-variable K-map



- Example: Simplify the Boolean function  
 $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$ .
- $F = A'C'D + ABC' + ABD + AB'C$ .

		$CD$			
		00	01	11	10
$AB$	00	0	1	0	0
	01	0	1	0	0
	11	1	1	1	0
	10	0	0	1	1

# Four-variable K-map

- Example: Simplify the Boolean function  
 $F = \sum(7, 9, 10, 11, 12, 13, 14, 15).$
- $F = AB + AC + AD + BCD.$


		$CD$			
		00	01	11	10
$AB$	00	0	0	0	0
	01	0	0	1	0
	11	1	1	1	1
	10	0	1	1	1

# Four-variable K-map



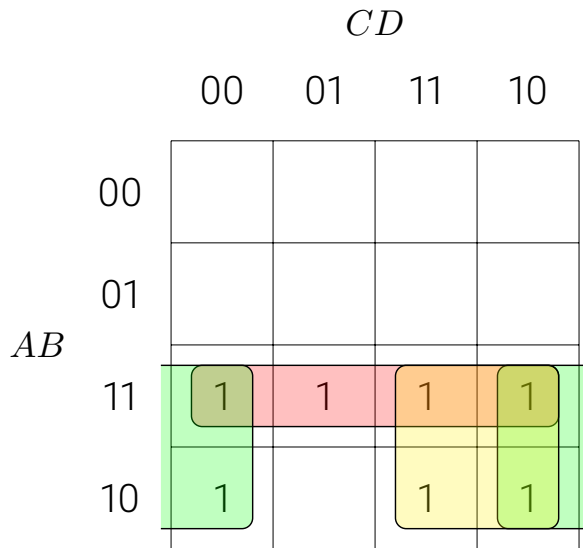- Example: Plot the logical expression  $F(A, B, C, D) = ABCD + AB'C'D' + AB'C + AB$  on a four-variable Karnaugh map.


$$\begin{aligned} F(A, B, C, D) &= ABCD + AB'C'D' + AB'C + AB \\ &= ABCD + AB'C'D' + AB'C(D + D') \\ &\quad + AB(C + C')(D + D') \\ &= \dots \\ &= \sum(8, 10, 11, 12, 13, 14, 15) \\ &= AB + AC + AD' \end{aligned}$$




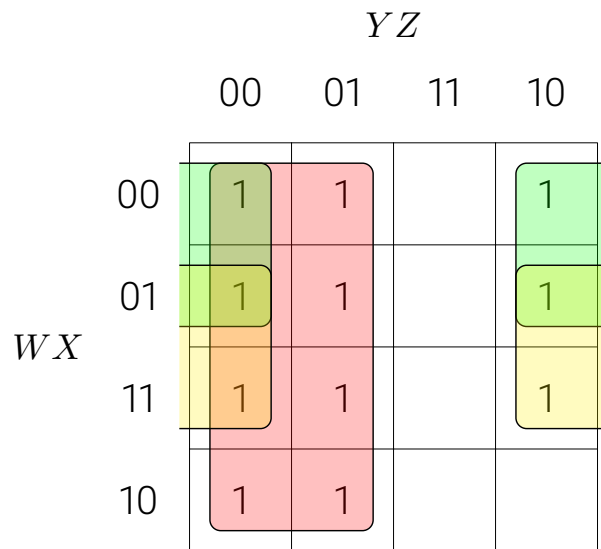
# Four-variable K-map

- Simplify the expression  $F(W, X, Y, Z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ .



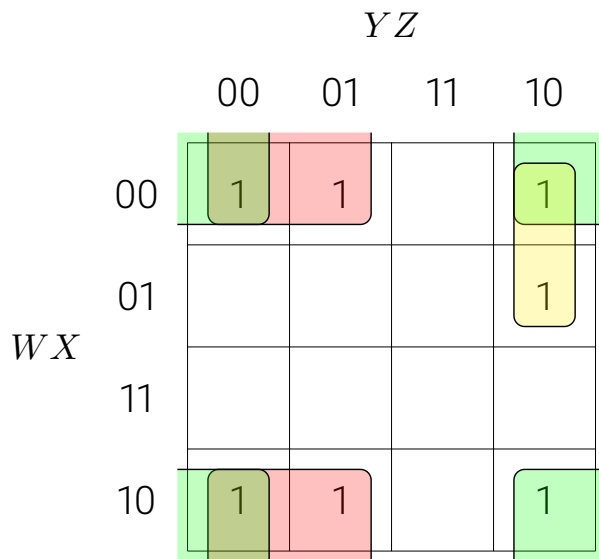
# Four-variable K-map



- Simplify the expression  $F(W, X, Y, Z) = W'X'Y' + X'YZ' + W'XYZ' + WX'Y'$ .

$$\begin{aligned} F(W, X, Y, Z) &= W'X'Y'(Z + Z') + X'YZ'(W + W') \\ &\quad + W'XYZ' + WX'Y'(Z + Z') \\ &= W'X'Y'Z + W'X'Y'Z' + WX'YZ' \\ &\quad + W'X'YZ' + W'XYZ' + WX'Y'Z \\ &\quad + WX'Y'Z' \\ &= \sum(0, 1, 2, 6, 8, 9, 10) \\ &= X'Y' + X'Z' + W'YZ' \end{aligned}$$



# Four-variable K-map



- Simplify the expression  
 $F(W, X, Y, Z) = \sum(3, 4, 5, 7, 9, 13, 14, 15)$ .
  - It may be noted that one quad can also be formed, but it is redundant as the squares contained by the quad are already covered by the pairs which are essential.
- $F = W'XY' + W'YZ + WY'Z + WXY$ .

		YZ			
		00	01	11	10
WX	00			1	
	01	1	1	1	
	11		1	1	1
	10		1		

# Four-variable K-map



- Simplify the expression  $F(W, X, Y, Z) = \prod(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$ .
  - The above expression is given in respect to the maxterms.
  - 0's are to be placed instead of 1's at the corresponding maxterm squares.
- $F' = Y' + XZ' \rightarrow F = Y(X' + Z)$ .

		YZ			
		00	01	11	10
WX	00	0	0	1	1
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	1

# Four-variable K-map



- Simplify the expression  $F(W, X, Y, Z) = \prod(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$ .
  - The other way to achieve the minimized expression is to consider the 1's of the Karnaugh map.
- $F = YZ + X'Y = Y(X' + Z)$ .

		YZ			
		00	01	11	10
WX	00	0	0	1	1
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	1

# Five-variable K-map



- Karnaugh maps with more than four variables are not simple to use.
  - The number of cells or squares becomes excessively large and combining the adjacent squares becomes complex.
  - A five-variable Karnaugh map contains  $2^5$  or 32 cells.

# Prime Implicants

- A *prime implicant* is a product term obtained by combining the maximum possible number of adjacent squares in the map.
- The prime implicants of a function can be obtained from the map by combining all possible maximum numbers of squares.
  - If a minterm in a square is covered by only one prime implicant, that prime implicant is said to be *essential*.
- Gate-level minimization:
  - Determine all essential prime implicants.
  - Find other prime implicants that cover remaining minterms.
  - Logical sum all prime implicants.



# Don't care conditions

- In practice, Boolean function is not specified for certain combinations of input variables.
  - Input combinations never occur during the process of a normal operation.
  - Those input conditions are guaranteed never to occur.
- Such input combinations are called *don't-care conditions*.
- These input combinations can be plotted on the Karnaugh map for further simplification.
  - The don't care conditions are represented by  $d$  or  $X$  in a K-map.
  - They can be either 1 or 0 upon needed.





# Don't care conditions

- Simplify the expression  $F(A, B, C, D) = \sum(1, 3, 7, 11, 15), d = \sum(0, 2, 5)$ .
- $F = A'B' + CD$ .

		$CD$			
		00	01	11	10
$AB$	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	

# Don't care conditions

- Simplify the expression  $F(A, B, C, D) = \sum(1, 3, 7, 11, 15), d = \sum(0, 2, 5)$ .
- $F = A'D + CD$ .

		$CD$			
		00	01	11	10
$AB$	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	

# Verilog user defined primitives



- Verilog has built-in primitives like gates, transmission gates, and switches.
  - This is a rather small number of primitives.
  - If we need more complex primitives, Verilog provides *User Defined Primitives* (UDP).
- UDP begins with reserve word `primitive` and ends with `endprimitive`.
  - Similar to what we do for module definition, ports/terminals of primitive should follow.
- **UDPs should be defined outside `module` and `endmodule`.**

```
1 primitive udp_syntax (a, b, c, d);  
2 output a;  
3 input b,c,d;  
4  
5 // UDP function code here  
6 endprimitive
```

# UDP ports rules



- An UDP can contain only one output and up to 10 inputs.
- Output port should be the first port followed by one or more input ports.
- All UDP ports are scalar, i.e. Vector ports are not allowed.
- UDPs can not have bidirectional ports.
- It is illegal to declare a `reg` for the output terminal of a combinational UDP.
- The output terminal of a sequential UDP requires an additional declaration as type `reg`.

# UDP body



- Functionality of primitive is described inside a `table`, and it ends with reserved word `endtable` as shown in the code below.

```
1 primitive udp_syntax (a, b, c);
2 output a;
3 input b,c;
4
5 // UDP function code here
6 // A = B | C;
7 table
8 //   B  C      : A
9     ?  1      : 1;
10    1  ?      : 1;
11    0  0      : 0;
12 endtable
13 endprimitive
```

# UDP body

- Table is used for describing the function of UDP.
- Each line inside a table is one condition.
  - When an input changes, the input condition is matched and the output is evaluated to reflect the new change in input.
  - An UDP cannot use **z** in the input table.
- UDP uses special symbols to describe functions like rising edge, don't care and so on.

# UDP body



Symbol	Interpretation	Explanation
?	0 or 1 or x	
b	0 or 1	
f	(10)	Falling edge on an input
r	(01)	Rising edge on an input
p	(01) or (0x) or (x1) or (1z) or (z1)	
n	(10) or (1x) or (x0) or (0z) or (z0)	
*	(??)	All transitions
-	-	No change