

A decorative graphic on the left side of the slide, consisting of a network of white lines and small circles on a teal background, resembling a circuit board or a stylized tree structure.

DIGITAL DESIGN

LAB10 SYNCHRONOUS SEQUENTIAL CIRCUIT



2021 FALL TERM @ CSE . SUSTECH

LAB10

- Synchronous sequential circuit
 - Latch
 - Flip Flops (key point of lab10)
- Verilog
 - `always@(posedge clk)` , `always@(negedge clk)` vs `always@*`
 - blocking assignment vs non-blocking assignment
- Practise

  4-2 PRIORITY-ENCODER IN LAB8(1)


```
//4-2 priority-encoder
module pri_encoder(
input I0, I1, I2, I3,
output reg [1:0] Y
);
always @* begin
    casex( {I3, I2, I1, I0})
        4'bxxx0: Y=2'b00;
        4'bxx01: Y=2'b01;
        4'bxx011: Y=2'b10;
        4'b0111: Y=2'b11;
    endcase
end
endmodule
```



If there is no 'default' branch and the branch(e.g. 4'b1111 in this demo) is not list in the branches of the 'case', the circuit state will remain unchanged, and then a **latch** will be generated to save the state.

LATCH

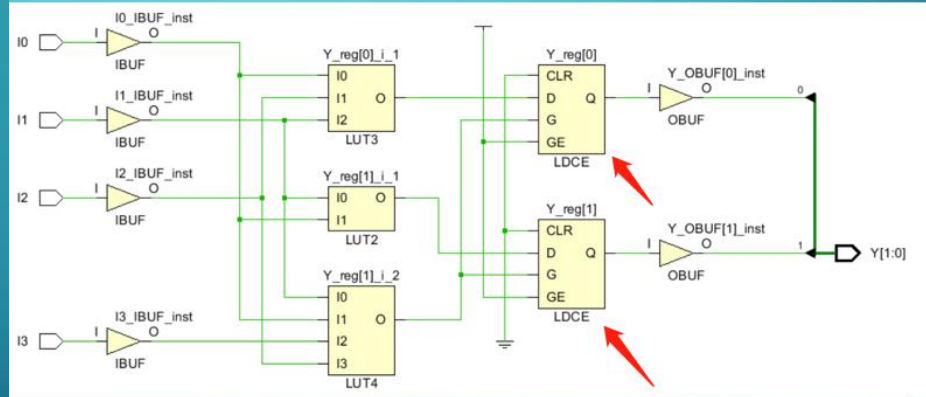
- The schematic on the right hand is the schematic of the synthesized design generated by vivado.
- LDCE**: transparent Data Latch with Asynchronous Clear and Gate Enable



For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

D LATCH

 - Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.




```
module D_Latch(  
    input En, D,  
    output reg Q,  
    output wire nQ  
);  
    assign nQ = ~Q;  
    always @*  
        if(En)  
            Q = D;  
        else  
            Q = Q;  
endmodule
```


D LATCH

- Schematic of RTL analysis:

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

 

- Simulation result of D Latch

 

FLIP FLOP

- The storage elements (memory) used in clocked sequential circuits are called **flipflops**.
- The most economical and efficient flip-flop constructed is the edge-triggered **D flipflop**, because it requires the smallest number of gates.

 


Figure for master-slave **negative-edge** triggered D flip-flop

```
module D_ff_from_latch(  
    input clk, D,  
    output Q  
);  
    wire Y, nq_master, nq_slaver;  
    /*...*/  
    D_Latch DL_master(clk, D, Y, nq_master);  
    D_Latch DL_slaver(~clk, Y, Q, nq_slaver);  
endmodule
```




D FLIP FLOP

- $Q^{n+1} = D$

```

 module D_flipflop(
input clk,D,
output reg Q,
output nQ
);
always @(posedge clk)
    Q <= D;
assign nQ = ~Q;
endmodule
    
```



CLK	Q
↑	D
0	no change
1	no change
↓	no change




JK FLIP FLOP(1)

- $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$

J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	$Q^{n'}$

JK		00	01	11	10
Q^n	0	0	0	1	1
	1	1	0	0	1

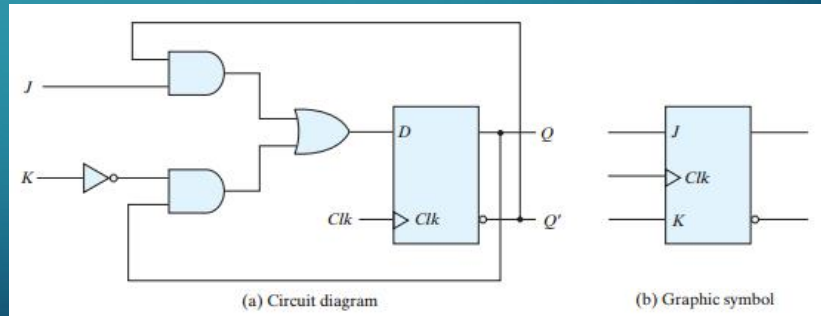

JK FLIP FLOP(2)

```

module J_K_Flip_Flop(
    input Clk, J, K,
    output reg Q,
    output nQ
);
    assign nQ = ~Q;
    always @ (posedge Clk)
        case ({J, K})
            2'b10: Q<= 1'b1; //set
            2'b01: Q<= 1'b0; //reset
            2'b11: Q<= nQ; //reverse
            2'b00: Q<= Q; //keep
        endcase
endmodule

```

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$


J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	Q^n



USING JK FLIP FLOP TO IMPLEMENT D FLIP FLOP

- JK Flip-Flop: $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$
- D Flip-Flop: $Q^{n+1} = D = D\overline{Q}^n + DQ^n$
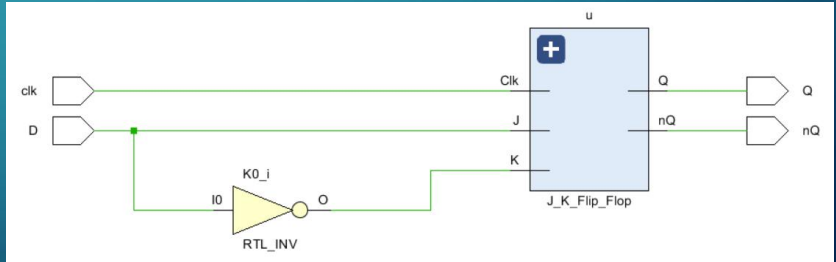
```
module Dff_byJKff(  
  input clk,D,  
  output Q,nQ  
);  
  J_K_Flip_Flop u(clk,D,~D,Q,nQ);  
endmodule
```




T FLIP FLOP


- The T (toggle) flip-flop is a complementing flip-flop, which can be obtained from a JK flip-flop when inputs J and K are tied together.

T	Q^{n+1}
0	Q^n
1	$\sim Q^n$
 
```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output nQ  
);  
    assign nQ = ~Q;  
    always @(posedge Clk)  
        case(T)  
            1'b1: Q <= ~Q;  
            1'b0: Q <= Q;  
        endcase  
endmodule
```


 
```
module Tff_by_JKff(  
    input Clk, T,  
    output Q, nQ  
);  
    J_K_Flip_Flop uT( Clk, T, T, Q, nQ);  
endmodule
```



WIRE VS REG(1)

There are two data types in Verilog: **wire** and **register**.

- **wire** is a kind of net, which is equivalent to physical connection.
- **wire** is used to connect two points, and thus does **not have any driving strength**
- **wire** data types can be used for connecting the output port to the actual driver
- a **wire** can be assigned a value by a continuous assign statement, which is used for **designing combinational logic**
- **default data type is wire**: this means that if you declare a port or variable without specifying reg or wire, it will be a 1-bit wide wire.
- **reg** is a kind of register, which is equivalent to memory cell.
- **reg** can **store value and drive strength**. **Reg** can be used for **modeling both combinational and sequential logic**.
- **reg** data type can be driven from initial and always block.
- **The LHS of a behavioral block(initial , always) should be declared as reg**
- **input port** could drive by both wire/register, but it could **ONLY** be declared as wire
- **output port** can be declared as wire or register, but it can **ONLY** drive wire
- **bidirectional port** can only be declared as wire

NON-BLOCKING ASSIGNMENT VS BLOCKING ASSIGNMENT

- The '=' token represents a **blocking procedural assignment**
- A **combinational logic always block** should use **Blocking assignments**("=").
- The '<=' token represents a **non-blocking procedural assignment**
- A **sequential logic always block** should use **Non-blocking assignments**("<=").

NOTE: DO NOT mixing blocking assignment and non-blocking assignment in the same always block !!!

PRACTICE(1)

- Try to construct a T flipflop with a reset input.
 - There would be a reset input port apart from other inputs(`clk`, `T`), while it enable the output of T flipflop is 1'b0, while it disable the circuit works as T flipflop
 - Do the design and verify the function of your design.
 - Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the minisys develop board.

PRACTICES(2)


$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

- Can this JK flip-flop work?
- Try to use it implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work? Explain the reason.

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
always @(posedge Clk)  
    if({J, K} == 2'b10) //set  
        begin  
            {Q, Qn} <= 2'b10;  
        end  
    else if ({J, K} == 2'b01) //reset  
        begin  
            {Q, Qn} = 2'b01;  
        end  
    else if ({J, K} == 2'b11) //reverse  
        begin  
            Q <= Qn;  
            Qn <= Q;  
        end  
    end  
endmodule
```


TIPS:

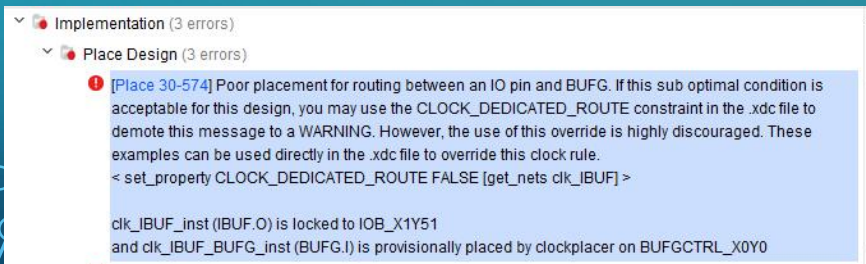- Constraints: if you want to use IO pin as clock, you should use the `CLOCK_DEDICATED_ROUTE` constraint in the .xdc file to demote the Error message to a WARNING.



```
set_property PACKAGE_PIN Y9 [get_ports clk]
set_property PACKAGE_PIN W9 [get_ports D]
set_property PACKAGE_PIN K17 [get_ports Q]
set_property PACKAGE_PIN L13 [get_ports Qn]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF]
```