

A decorative graphic on the left side of the slide, consisting of a network of white lines and small circles on a teal background, resembling a circuit board or a neural network.

DIGITAL DESIGN

LAB9 COMBINATORIAL CIRCUIT3

2021 FALL TERM @ CSE . SUSETCH

LAB9

- Combinational circuit(3)
 - Multiplexer
 - Demultiplexer
- Practice

MULTIPLEXER

- a **Multiplexer** (or **mux**) is a device that selects one of several input signals and forwards the selected input to the output.
- A multiplexer of 2^n inputs has n select lines. Select lines are used to select one of the input line to be sent to the output.
- Multiplexers are mainly used to increase the amount of data that can be sent over the network within a certain amount of time and bandwidth. A multiplexer is also called a **data selector**.
- Multiplexers can also be used to implement Boolean functions of multiple variables.


MULTIPLEXER

$$Y = m_0 \cdot D_0 + m_1 \cdot D_1 + m_2 \cdot D_2 + m_3 \cdot D_3$$

$$Y = (s_1' \cdot s_0') \cdot D_0 + (s_1' \cdot s_0) \cdot D_1 + (s_1 \cdot s_0') \cdot D_2 + (s_1 \cdot s_0) \cdot D_3$$

selection input		output
s1	s0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

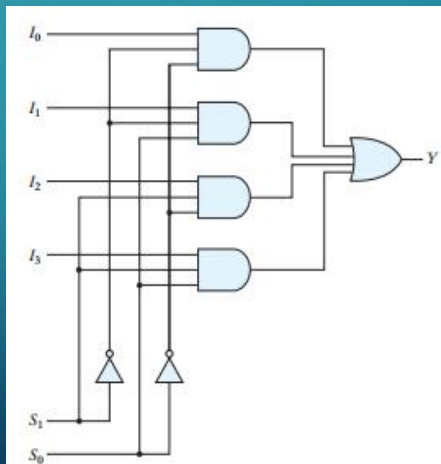function table for 4-to-1-line
multiplexer



Here I0 is the D0, I1 is the D1, I2 is the D2, I3 is the D3.

s1 is the MSB of the select lines, s0 is the LSB of the select lines.

MULTIPLEXER

$$Y = m_0.D_0 + m_1.D_1 + m_2.D_2 + m_3.D_3$$

$$Y = (s1'.s0').D0 + (s1'.s0).D1 + (s1.s0').D2 + (s1.s0).D3$$

selection input		output
s1	s0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

function table for 4-to-1-line
multiplexer

```
module multiplexer(  
    input w,  
    input x,  
    input y,  
    input z,  
    input [1:0] s, //select  
    output reg o  
);  
always @*  
begin  
    case (s)  
        2'b00: o = w;  
        2'b01: o = x;  
        2'b10: o = y;  
        2'b11: o = z;  
    endcase  
end  
endmodule
```

Here w is the D0, x is the D1, y is the D2, z is the D3.

s1 is the MSB of the select lines, s0 is the LSB of the select lines.

MULTIPLEXER

$$Y = m_0 \cdot D_0 + m_1 \cdot D_1 + m_2 \cdot D_2 + m_3 \cdot D_3$$


$$Y = (s_1' \cdot s_0') \cdot D_0 + (s_1' \cdot s_0) \cdot D_1 + (s_1 \cdot s_0') \cdot D_2 + (s_1 \cdot s_0) \cdot D_3$$

selection input		output
s1	s0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

function table for 4-to-1-line
multiplexer

```

 module multiplexer_tb();
    reg sI0, sI1, sI2, sI3;
    reg [1:0]sS;
    wire sY;
    multiplexer u(sI0, sI1, sI2, sI3, sS, sY);
    initial
    begin
        {sS, sI3, sI2, sI1, sI0} = 6'b000000;
        repeat(63) #10 {sS, sI3, sI2, sI1, sI0} = {sS, sI3, sI2, sI1, sI0} + 1;
        #10 $finish;
    end
endmodule
    
```




MULTIPLEXER(74151:8-TO-1-LINE MULTIPLEXER)

```

module multiplexer74151( EN,S2,S1,S0,D7,D6,
D5,D4,D3, D2,D1,D0,Y,W);
    input EN, S2, S1,S0, D7, D6, D5,
        D4, D3, D2, D1, D0;
    output reg Y;
    output W;
    always @*
    if (~EN)
        case ({S2,S1,S0})
            3'b000: Y = D0;
            3'b001: Y = D1;
            3'b010: Y = D2;
            3'b011: Y = D3;
            3'b100: Y = D4;
            3'b101: Y = D5;
            3'b110: Y = D6;
            3'b111: Y = D7;
        endcase
    else
        Y = 1'b0;
    assign W=~Y;
endmodule
    
```

inputs				output	
EN	S2	S1	S0	Y	W
1	X	X	X	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

function table for 74151

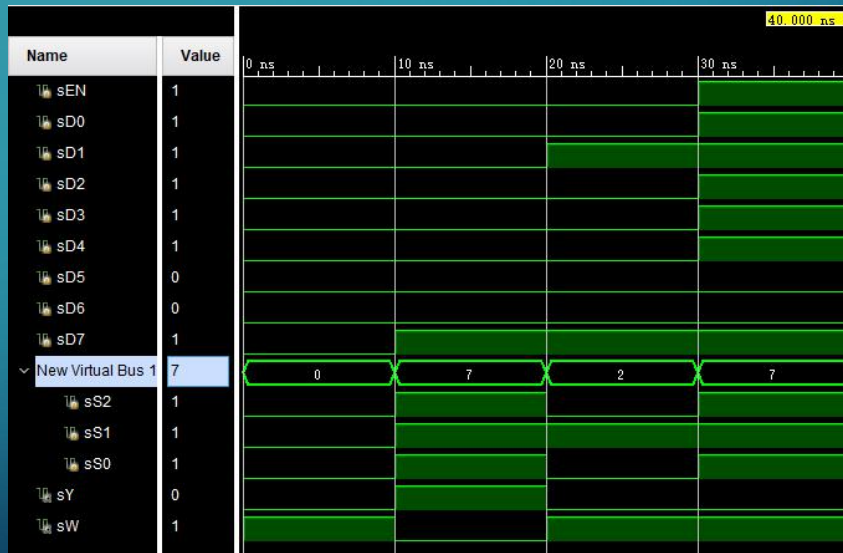

AB/00/01/10/11

MULTIPLEXER (IMPLEMENT BOOLEAN FUNCTIONS-1)

- Use 74151 implement the following logic function.

$$\begin{aligned}
 F(A, B, C) &= \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC \\
 &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}BC + ABC + \overline{A}BC \\
 &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}BC + ABC \\
 &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC \\
 &= m_0 \cdot 1 + m_1 \cdot 0 + m_2 \cdot 1 + m_3 \cdot 1 + m_4 \cdot 1 + m_5 \cdot 0 + m_6 \cdot 0 + m_7 \cdot 1 \\
 Y &= m_0 \cdot D_0 + m_1 \cdot D_1 + m_2 \cdot D_2 + m_3 \cdot D_3 + m_4 \cdot D_4 + m_5 \cdot D_5 + m_6 \cdot D_6 + m_7 \cdot D_7
 \end{aligned}$$



MULTIPLEXER(IMPLEMENT BOOLEAN FUNCTIONS-2)

```
module multiplexer74151( EN,S2,S1,S0,D7,D6,D5,D4,D3, D2,D1,D0,Y,W);  
    input EN, S2, S1,S0, D7, D6, D5,  
        D4, D3, D2, D1, D0;  
    output reg Y;  
    output W;  
    always @*  
    if (~EN)  
        case ({S2,S1,S0})  
            3'b000: Y = D0;  
            3'b001: Y = D1;  
            3'b010: Y = D2;  
            3'b011: Y = D3;  
            3'b100: Y = D4;  
            3'b101: Y = D5;  
            3'b110: Y = D6;  
            3'b111: Y = D7;  
        endcase  
    else  
        Y = 1'b0;  
        assign W=~Y;  
    endmodule
```

$$F(A,B,C) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC$$

```
module fun_a_b_c(input A,B,C,output F);  
    assign F=( (~A)&(~C) ) | ( (~B)&(~C) ) | ((~A)&B) | (B&C);  
endmodule
```

$$F(A,B,C) = m_0.1 + m_1.0 + m_2.1 + m_3.1 + m_4.1 + m_5.0 + m_6.0 + m_7.1$$

```
module fun_a_b_c_use_mux(input A,B,C, output F);  
    wire sen,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0;  
    wire snf;  
  
    assign {sen,sd7,sd5,sd4,sd3,sd2,sd1,sd0}= 9'b0_1001_1101;  
  
    multiplexer74151 u74151(.EN(sen),  
        .S2(A),.S1(B),.S0(C),  
        .D7(sd7),.D6(sd6),.D5(sd5),.D4(sd4),.D3(sd3),.D2(sd2),.D1(sd1),.D0(sd0),  
        .Y(F),.W(snf));  
endmodule
```

MULTIPLEXER(IMPLEMENT BOOLEAN FUNCTIONS-3)

```
timescale 1ns / 1ps
//////////////////////////////////////////////////////////////////...
module fun_abc_sim();
  reg sa, sb, sc;
  wire sf, sf_mux;
  fun_a_b_c uf(.A(sa),.B(sb),.C(sc),.F(sf));
  fun_a_b_c_use_mux uf_mux(.A(sa),.B(sb),.C(sc),.F(sf_mux));
  /*...*/
  initial
  begin
    {sa, sb, sc} = 3'b000;
    repeat(7)
    begin
      #100 {sa, sb, sc} = {sa, sb, sc} + 1;
      $display($time, " {sa, sb, sc}=%d_%d_%d sf=%d sf_mux=%d", sa, sb, sc, sf, sf_mux);
    end
    #100 $finish();
  end
endmodule
```

$$F(A, B, C) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}B + BC$$

```
100{sa, sb, sc}=0_0_1 sf=1 sf_mux=1
200{sa, sb, sc}=0_1_0 sf=0 sf_mux=0
300{sa, sb, sc}=0_1_1 sf=1 sf_mux=1
400{sa, sb, sc}=1_0_0 sf=1 sf_mux=1
500{sa, sb, sc}=1_0_1 sf=1 sf_mux=1
600{sa, sb, sc}=1_1_0 sf=0 sf_mux=0
700{sa, sb, sc}=1_1_1 sf=0 sf_mux=0
$finish called at time : 800 ns : File "D:/xilinx_wor
```

DE-MULTIPLEXER


- a **De-multiplexer** (or **De-mux**) is a device taking a single input signal and selecting one of many data-output-lines, which is connected to the single input.

selection input		output			
S1	S0	Y3	Y2	Y1	Y0
0	0	0	0	0	D
0	1	0	0	D	0
1	0	0	D	0	0
1	1	D	0	0	0

function table of 1-to-4 de-multiplexer
D is the data input

```
module demultiplexer(  
    input D,  
    input [1:0] S,  
    output reg Y0,  
    output reg Y1,  
    output reg Y2,  
    output reg Y3  
)  
    always@*  
    begin  
        case (S)  
            2'b00: {Y3, Y2, Y1, Y0}={1'b0, 1'b0, 1'b0, D};  
            2'b01: {Y3, Y2, Y1, Y0}={1'b0, 1'b0, D, 1'b0};  
            2'b10: {Y3, Y2, Y1, Y0}={1'b0, D, 1'b0, 1'b0};  
            2'b11: {Y3, Y2, Y1, Y0}={D, 1'b0, 1'b0, 1'b0};  
        endcase;  
    end  
endmodule
```
 
```
module demultiplexer_tb();  
    reg [1:0] sS;  
    reg sD;  
    wire sY0, sY1, sY2, sY3;  
    demultiplexer u(sD, sS, sY0, sY1, sY2, sY3);  
    initial  
    begin  
        {sD, sS} = 3'b000;  
        repeat(7) #10 {sD, sS} = {sD, sS}+1;  
        #10 $finish;  
    end  
endmodule
```



PRACTICES

1. Use 74151(8-to-1-line multiplexer) realize the following logic function

$$Y = A'B'C'D' + BC'D + A'C'D + A'BCD + ACD$$

$$= A'B'C'D' + A'BC'D + ABC'D + A'B'C'D + A'BC'D + A'BCD + ABCD + AB'C'D$$

- Do the design and verify the function of your design.
- Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the minisys develop board.

$$= m_0 + m_1 + m_5 + m_7 + m_{13} + m_{15}$$

2. Is there any relationship between Decoder and De-mux?

3. Please try to implement a 1-4 De-mux by using a 2-4 Decoder