

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a teal background, resembling a circuit board or a stylized tree structure.

DIGITAL DESIGN

LAB12 FREQUENCY DIVIDER

2021 FALL TERM @ CSE . SUSTECH

LAB12

- Frequency divider
 - Divide by even
 - Divide by odd
- Structure design
 - demo
 - Flowing light
 - 7-seg tube

CLOCK ON MINISYS BOARD

- **Minisys** board includes a **100MHz** crystal oscillator connected to the main chip **Y18** pin. Through requirement design, the input clock can drive MMCMs or PLLs to produce multi-frequency clock and phase changes.

FREQUENCY DIVIDER

- A **Frequency Divider**, also called a **clock divider** or scaler or pre-scaler, is a circuit that takes an input signal of a frequency f_{in} , and generates an output signal of a frequency f_{out} :

$$f_{out} = f_{in}/n \text{ (n is an integer).}$$

- For power-of-2 integer division, a simple binary counter can be used, clocked by the input signal. The least-significant output bit alternates at $1/2$ the rate of the input clock, the next bit at $1/4$ the rate, the third bit at $1/8$ the rate, etc.
- An arrangement of flipflops is a classic method for integer-n division. Such division is frequency and phase coherent to the source over environmental variations including temperature. The easiest configuration is a series where each flip-flop is a divide-by-2. For a series of three of these, such system would be a divide-by-8. By adding additional logic gates to the chain of flip flops, other division ratios can be obtained. Integrated circuit logic families can provide a single chip solution for some common division ratios.

FREQUENCY DIVIDER(N:4)

```
* timescale 1ns / 1ps
module clk_div(input clk,rst_n,output reg clk_out);
    parameter period = 4;
    reg [3:0] cnt;
    always@(posedge clk, negedge rst_n)
    begin
        if(~rst_n)begin
            cnt <=0;
            clk_out<=0;
        end
        else
            if(cnt==((period>>1) - 1)) begin
                clk_out <= ~clk_out;
                cnt <=0;
            end
            else begin
                cnt <= cnt+1;
            end
        end
    end
endmodule
```

```
* timescale 1ns / 1ps

module clk_div_tb( );
    reg clk,rst_n;
    wire clk_out;
    clk_div cd(clk,rst_n,clk_out);
    initial fork
        clk <=0;
        rst_n <=0;
        # 3 rst_n <= 1;
        forever
            #5 clk = ~clk;
    join
endmodule
```



FREQUENCY DIVIDER(N:5)

```

`timescale 1ns / 1ps
module clock_div(input clk,rst_n,output reg clk_out );
//reg [25:0]cnt;...
reg [2:0] step1,step2;
always@(posedge clk)begin
    if(~rst_n)begin
        step1<=3'b000;
    end
    else begin
        case(step1)
            3'b000: step1<=3'b001;
            3'b001: step1<=3'b011;
            3'b011: step1<=3'b100;
            3'b100: step1<=3'b010;
            3'b010: step1<=3'b000;
            default:step1<=3'b000;
        endcase
    end
end
end

```

```
assign clk_out=step1[0]|step2[0];
```

```

always @(negedge clk,negedge rst_n)
    if(~rst_n)
        step2<=3'b000;
    else
        case(step2)
            3'b000: step2<=3'b001;
            3'b001: step2<=3'b011;
            3'b011: step2<=3'b100;
            3'b100: step2<=3'b010;
            3'b010: step2<=3'b000;
            default:step2<=3'b000;
        endcase
    end
endmodule

```

```

`timescale 1ns / 1ps
////////////////////////////////////

module clock_div_tb( );
reg clk,rst_n;
wire clk_out;
clock_div cd(clk,rst_n,clk_out);
initial fork
    clk <=0;
    rst_n <=0;
    # 3 rst_n <= 1;
    forever
        #5 clk = ~clk;
join
endmodule


```



DEMO1 (FLOWING LIGHT1)

```
timescale 1ns / 1ps
module flowing_light_lite(input clk,rst_n,output[7:0] led);
    reg [7:0] light_reg;
    always@(posedge clk,negedge rst_n)
    begin
        if(!rst_n)
            light_reg<=8'b0000_0001;
        else if(light_reg == 8'b1000_0000)
            light_reg<=8'b0000_0001;
        else
            light_reg<=light_reg<<1;
        end
    assign led = light_reg;
endmodule
```
 
```
timescale 1ns / 1ps
module flow_water_tb();
    reg clk,rst_n;
    wire [7:0]led;
    //flow_water_lights fs(clk,rst_n,led,cnt,ns);
    flowing_light_lite fs(clk,rst_n,led);
    initial fork
        rst_n <=1'b0;
        clk <= 1'b0;
        #2 rst_n <=1'b1;
        forever
            #5 clk = ~clk;
        join
    endmodule
```



DEMO1 (FLOWING LIGHT2)

Minisys board includes a 100MHz crystal oscillator connected to the main chip Y18 pin.


```
`timescale 1ns / 1ps
module flash_led_top(
    input clk,
    input rst_n,
    input sw0,
    output [7:0]led
);

    wire clk_bps;
    counter counter(
        .clk( clk ),
        .rst_n( rst_n ),
        .clk_bps( clk_bps )
    );
    flash_led_ctl flash_led_ctl(
        .clk( clk ),
        .rst_n( rst_n ),
        .dir( sw0 ),
        .clk_bps( clk_bps ),
        .led( led )
    );
endmodule
```

```
`timescale 1ns / 1ps
module counter(
    input clk,
    input rst,
    output clk_bps
);
    reg [13:0]cnt_first,cnt_second;
    always @( posedge clk or posedge rst )
        if( rst )
            cnt_first <= 14'd0;
        else if( cnt_first == 14'd10000 )
            cnt_first <= 14'd0;
        else
            cnt_first <= cnt_first + 1'b1;
    always @( posedge clk or posedge rst )
        if( rst )
            cnt_second <= 14'd0;
        else if( cnt_second == 14'd10000 )
            cnt_second <= 14'd0;
        else if( cnt_first == 14'd10000 )
            cnt_second <= cnt_second + 1'b1;
    assign clk_bps = cnt_second == 14'd10000 ? 1'b1 : 1'b0;
endmodule
```

```
module flash_led_ctl(
    input clk,
    input rst_n,
    input dir,
    input clk_bps,
    output reg[7:0]led
);
    always @( posedge clk or negedge rst_n )
        if( !rst_n )
            led <= 8'h80;
        else
            case( dir )
                1'b0: //从左向右
                    if( clk_bps )
                        if( led != 8'd1 )
                            led <= led >> 1'b1;
                    else
                        led <= 8'h80;
                1'b1: //从右向左
                    if( clk_bps )
                        if( led != 8'h80 )
                            led <= led << 1'b1;
                    else
                        led <= 8'd1;
            endcase
endmodule
```


DEMO1 (FLOWING LIGHT2)

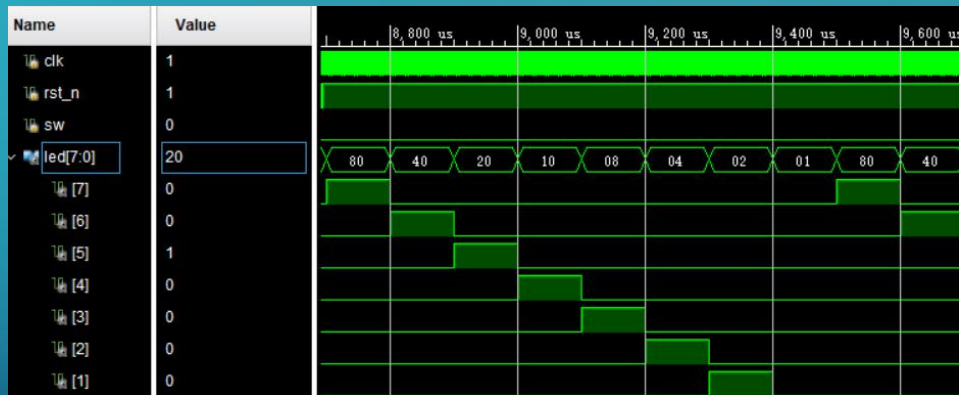

Test on Minisys board



```
set_property PACKAGE_PIN Y18 [get_ports clk]
```

DEMO2 : 7-SEG TUBE



```
always @( posedge clk or negedge rst) //frequency division : clk->clkout...

always @(posedge clkout or negedge rst) //change scan_cnt based on clkout    ...

always @( scan_cnt)                //select tube...

always @ (scan_cnt ) //decoder to display on 7-seg tube...
```

```
module scan_seg ( rst ,clk ,DIG ,Y );
    input rst ://reset
    input clk ://system clock 100MHz
    output [7:0] DIG ://bit selection
    output [7:0] Y :// seg selection

    reg clkout : //
    reg [31:0] cnt;
    reg [2:0] scan_cnt ;

    parameter period= 200000://500HZ stable
    //parameter period= 250000://400HZ stable
    //parameter period= 5000000://20HZ loop one by one
    //parameter period= 2500000://40HZ twenkle
    //parameter period= 1000000://100HZ twenkle

    reg [6:0] Y_r;
    reg [7:0] DIG_r;
    assign Y = {1'b1, (~Y_r[6:0])}; //dot never light
    assign DIG = ~DIG_r;
```

DEMO2 : 7-SEG TUBE

```
always @(posedge clk or negedge rst) //frequency division : clk->clkout
begin
    if (!rst) begin
        cnt <= 0;
        clkout <=0;
    end
    else begin
        if (cnt == (period >> 1) - 1)
            begin
                clkout <= ~clkout;
                cnt<=0;
            end
        else
            cnt<= cnt+1;
        end
    end
end
```

```
always @( scan_cnt) //select tube
begin
    case ( scan_cnt )
        3'b000 : DIG_r = 8'b0000_0001;
        3'b001 : DIG_r = 8'b0000_0010;
        3'b010 : DIG_r = 8'b0000_0100;
        3'b011 : DIG_r = 8'b0000_1000;
        3'b100 : DIG_r = 8'b0001_0000;
        3'b101 : DIG_r = 8'b0010_0000;
        3'b110 : DIG_r = 8'b0100_0000;
        3'b111 : DIG_r = 8'b1000_0000;
        default :DIG_r = 8'b0000_0000;
    endcase
end
```

```
always @(posedge clkout or negedge rst) //change scan_cnt based on clkout
begin
    if (!rst)
        scan_cnt <= 0 ;
    else begin
        scan_cnt <= scan_cnt + 1;
        if(scan_cnt==3'd7) scan_cnt <= 0;
    end
end
```

```
always @ (scan_cnt ) //decoder to display on 7-seg tube
begin
    case (scan_cnt)
        0: Y_r = 7'b0111111; // 0
        1: Y_r = 7'b0000110; // 1
        2: Y_r = 7'b1011011; // 2
        3: Y_r = 7'b1001111; // 3
        4: Y_r = 7'b1100110; // 4
        5: Y_r = 7'b1101101; // 5
        6: Y_r = 7'b1111101; // 6
        7: Y_r = 7'b0100111; // 7
        8: Y_r = 7'b1111111; // 8
        9: Y_r = 7'b1100111; // 9
        10: Y_r = 7'b1110111; // A
        11: Y_r = 7'b1111100; // b
        12: Y_r = 7'b0111001; // c
        13: Y_r = 7'b1011110; // d
        14: Y_r = 7'b1111001; // E
        15: Y_r = 7'b1110001; // F
        default: Y_r = 7'b0000000;
    endcase
end
```

PRACTICE

- 1. Implement a 'Breathing lamp' on Minsys board, the 'Breathing lamp' here is a led which light on for 1 seconds while light off for 1 seconds.
- 2. implement a Rolling subtitles showing 'CSE' and flowing from right to left on the tube of Minisys board.

TIPS

If you have any problem about frequency divider, wish this demo will help you.
2-stages is an easier way for understanding sequential circuit compared to 1-stage.

```
module clk_div_2(input clk,rst_n,output reg clk_out );  
  
    parameter period=4;  
    reg [3:0] cnt;  
    reg [3:0] cnt_ns;  
    reg clk_out_ns;  
    always@(posedge clk,negedge rst_n)...  
  
    always@(*)begin...  
  
    always@(posedge clk,negedge rst_n)...  
  
    always@(*)...  
endmodule
```

```
always@(posedge clk,negedge rst_n)  
begin  
    if(~rst_n)begin...  
    else  
        clk_out<=clk_out_ns;  
    end  
  
    always@(*)begin  
    if(~rst_n)  
        clk_out_ns = 1;  
    else  
        if(cnt==((period>>1)-1))  
            clk_out_ns = ~clk_out;  
        else  
            clk_out_ns = clk_out_ns;  
        end  
end
```

```
always@(posedge clk,negedge rst_n)  
begin  
    if(~rst_n)begin  
        cnt<=0;  
    end  
    else begin  
        cnt<=cnt_ns;  
    end  
end  
  
always@(*)  
begin  
    if(cnt==((period>>1)-1))  
        cnt_ns=0;  
    else  
        cnt_ns=cnt+1;  
    end  
end
```

